

Problems in Old Midterm 1 Exam

To receive credits show all your work clearly. Write only answer gets 0.

1. Number system and conversion

1a.1) Convert 155 to

- a) **Binary** number and
- b) **Hexadecimal** number

1a.2) Convert 764 in octal-based number (base-8) to


- a) **Binary** number and
- b) **Hexadecimal** number

1b) Find a **binary number** of a given *decimal* number **456**


1c) Find **hexadecimal number** of a given *octal (based-8)* number **6471₈**

2) Given the circuit implemented with transistors, choose (circle) the one that implements the logic 2-input **NOR gate**.


(a)

 


(b)

 

(c)

 

(d)

 

- 3) Which of the following is the correct Boolean equation for **output d12 of a 4x16 decoder**?

Note: inputs are in the order i3 i2 i1 i0 and outputs are in the order of d15 d14 ... d1 d0

- (a) $d_{12} = i_3 + i_2 + i_1' + i_0$ (b) $d_{12} = i_3 + i_2 + i_1' + i_0'$
(c) $d_{12} = i_3 i_2 i_1' i_0$ (d) $d_{12} = i_3' i_2' i_1 i_0'$
(e) $d_{12} = i_3' i_2' i_1 i_0$ (f) $d_{12} = i_3 i_2 i_1' i_0'$

- 4) Given a 4x2 **priority encoder** (where **d3 has the highest priority** and inputs are in the order d3 d2 d1 d0), what is the output of e1 and e0 given that d0 = 1, d1 = 0, **d2 = 1**, d3 = 0.

- (a) e1 = 0, e0 = 0 (b) e1 = 0, e0 = 1
(c) e1 = 1, e0 = 0 (d) e1 = 1, e0 = 1
(e) The output is unknown since the input combination is invalid for a priority encoder.

- 5) Given $F(a, b, c) = ac + b'c$, which of the following is the **inverse of F**?


- (a) $F' = c'$ (b) $F' = a'c' + b$
(c) $F' = a'b + c'$ (d) $F' = a'c' + bc'$
(e) $F' = a'b + c$
(f) None of the above

- 6) Given the following logic equation

$$F = A'B' + A'BC' + B'C + A(B+C)'$$

Minimize/Simplify using *only Boolean algebra*.

 7) Given the following circuit using **3x8 decoder** and **4-input OR gate**, write the Boolean equation/expression in a **sum-of-minterm** form.




8) Given the following Boolean equation:

$$F(c, d, a, b) = \Sigma(0, 2, 6, 7, 8, 10, 12, 14)$$

8a) Use Karnaugh-map to find its **minimal** sum-of-product form.

 
8b) Implement the given equation $F(c, d, a, b)$ using 4x1 MUX with signals a and b connecting to select lines S1 and S0, respectively.



9) Write the **simplified/minimized sum-of-products** form for F using **K-map**

$$F = (x + y + w')(x' + y' + z)(x' + w + z')$$

 - 10) Given a digital circuit below, implement the circuit above using **only 2-input NAND gates**. Eliminate unnecessary NAND gates.




- 11) Using the combinational logic design process, design a circuit with two 2-bit inputs (A and B) and one 2-bit output (M). Your circuit should output the **minimum** of the two input values. For example,

- $A = a_1a_0 = 10$ and $B = b_1b_0 = 11$, then $M = m_1m_0 = 10$
since $10 (= 2 \text{ in decimal}) < 11 (= 3 \text{ in decimal})$
- $A = a_1a_0 = 11$ and $B = b_1b_0 = 01$, then $M = m_1m_0 = 01$
- $A = 10$ and $B = 10$, then $M = 10$ since both inputs are the same value

Your answers must include

- a) **Truth table**
- b) **minimized** sum-of-products form for the outputs

 - 12) Consider four seats arranged in a circle and described by **Boolean variables** i_0 to i_3 .



Boolean variable i_0 is true ($=1$) if seat 0 is occupied and i_0 is false if the seat is not occupied (no one is sitting in the seat), likewise for i_1 , i_2 , and i_3 .


- a) Write a **truth table** that is true ($F = 1$) if **at least two people are sitting next to each other** and **at least one seat is not occupied**.

- b) Simplify your design using K-map. Write the expression/equation in minimal sum-of-product form.


- 13) A "2-bit" comparator circuit receives **two 2-bit numbers**, $A = A_1A_0$, and $B = B_1B_0$. Design this comparator that produces an output $F = 1$ if $A \geq B$.
Write its minimum sum-of-product form.

14) Given the following circuit,


 
a) write its *minimized sum-of-products form* for F



 
b) Implement the simplified equation of F from 14a) using 4x1 MUX with signals b and c connecting to select lines S1 and S0, respectively, as shown below.



  15) Given a level-sensitive SR Latch with the input pattern below, complete the timing diagram below (draw S1, R1, and Q). Assuming that S1, R1, and Q are initially 0 and the logic gates have a *very small* nonzero delay.




 16) Given the following waveform where C and D are inputs and the rest are outputs, which output waveform (Q1, Q2, Q3, Q4, or Q5) belongs to



D-FF using rising edge of Clk


Choose one of Q1, Q2, Q3, Q4, Q5

 

Note: **C** and **D** in the **above waveform** are connected to **Clk** and **D**, respectively of this flip-flop.



D-latch with the function table below

Choose one of Q1, Q2, Q3, Q4, Q5

 


Note: **C** and **D** in the **above waveform** are connected to **C** and **D**, respectively of this latch.

  17) Given a level-sensitive SR Latch with the input pattern below, complete the timing diagram below (draw S1, R1, and Q). Assuming that S1, R1, and Q are initially 0




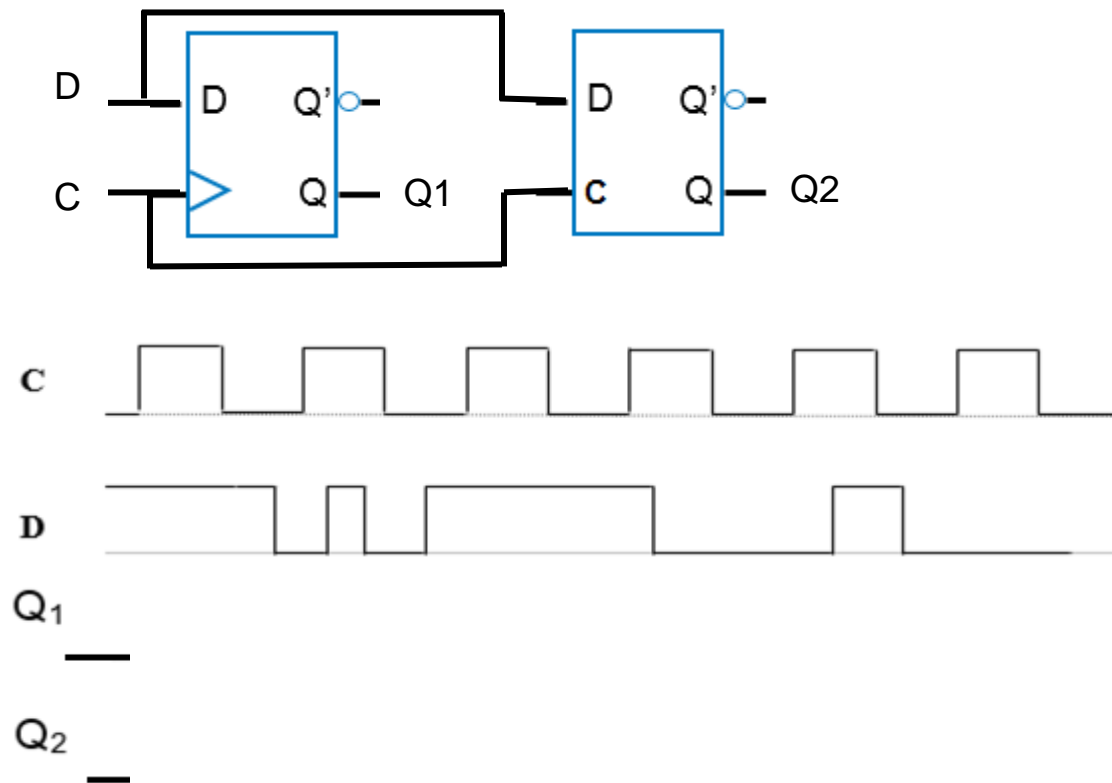18) Trace the behavior of **D-Latch** and **D flip-flop** for the following input patterns. Assume that Q_1 and Q_2 is initially 0 and logic gates have a very small nonzero delay.



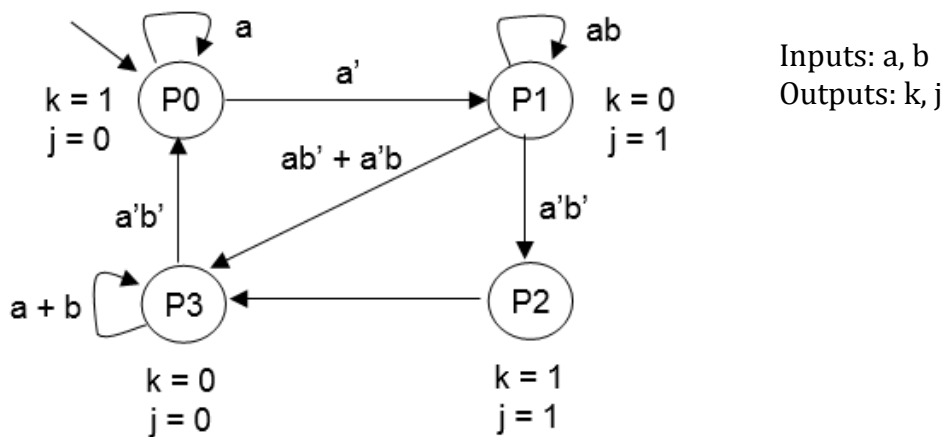19) Using the **sequential logic design process**, convert the provided state diagram (FSM) to **a circuit**. Be sure to label and show each step.

Note: Write the Boolean equations (in minimum sum-of-products form) is sufficient. NO need to draw a circuit.




20) Design a synchronous sequential circuit of a sequence detector, which has one input b and one output w . It accepts a sequence of bits (one bit (0 or 1) at a time) and outputs $w = 1$ when the **target sequence 1001** is detected. **Non-Overlapping** sequence is detected.

a) Draw its **state diagram**

b) **Minimum of bits** to represent/encode states in your designed state diagram are _____

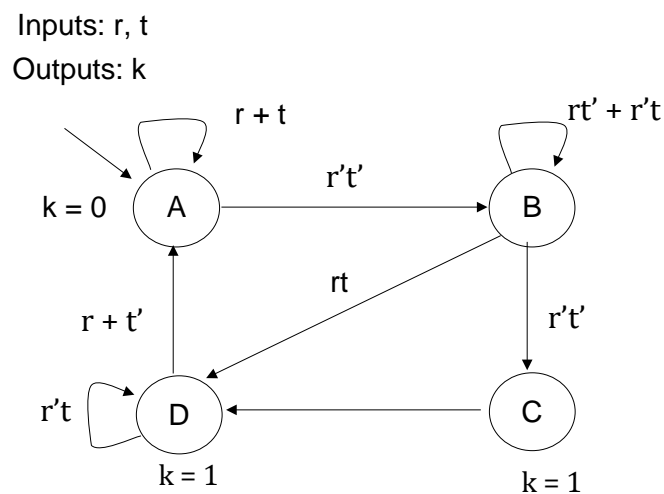21) Using the sequential logic design process, convert the provided state diagram (FSM) to a circuit. Be sure to label and show each step.

Note: Write the Boolean equations (in minimum sum-of-products form) is sufficient. You DO NOT need to provide a gate-level implementation (no drawing a circuit).



22) Design a vending machine that **delivers coffee after depositing 35 cents**.

There is a single coin slot for two types of coins, N and D.

D is for dimes (10 cents) and N is for nickels (5 cents).

It does not take other coin types. Single coin slot means that you can insert one coin at a time!

If a dime is deposited, D is 1 and N is 0.

If a nickel is deposited N is 1, D is 0.

N and D cannot be 1 at the same time.

The vending machine does **not** return changes if you deposit more than 35 cents.

When 35 cents is reached, coffee is served by outputting S as 1 that enables the coffee dripping system. **In the next cycle, the vending machine goes back to the initial state for the next coin input for another coffee.**

a) Draw a state diagram (FSM).

b) From your state diagram, what are the minimum of bits that your design needs to use for a state register?

