 
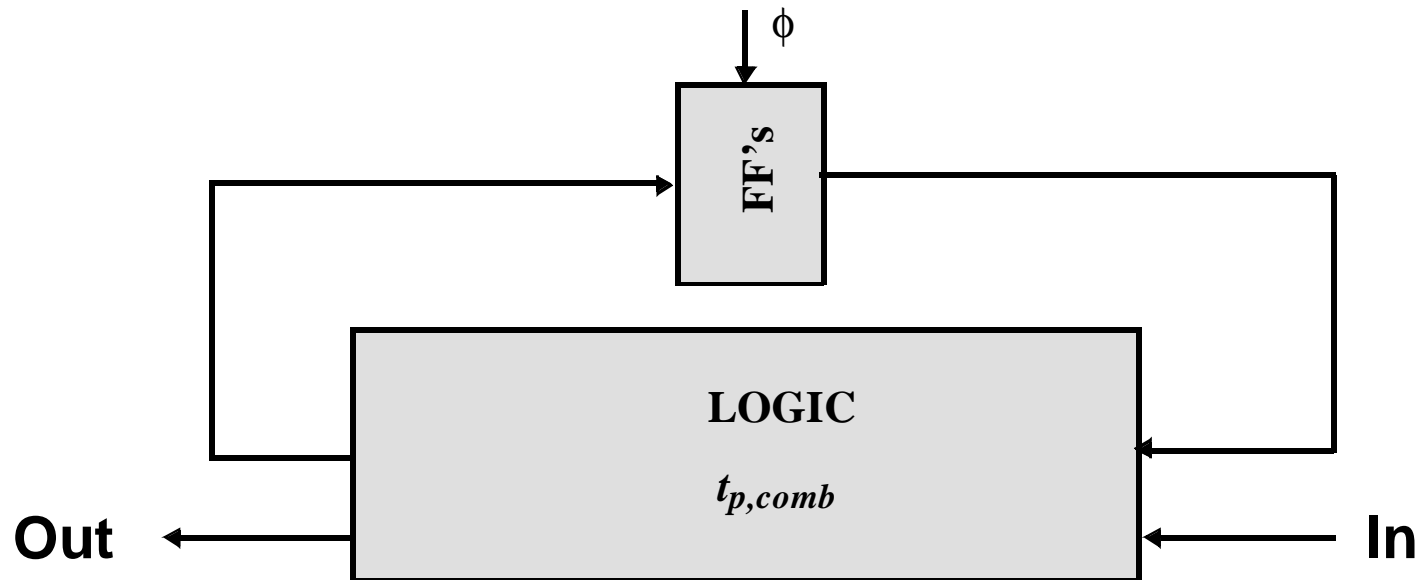

SEQUENTIAL LOGIC




Sequential Logic





2 storage mechanisms

- **positive feedback**
- **charge-based**

Positive Feedback: Bi-Stability


 


Meta-Stability

 
 


Gain should be larger than 1 in the transition region

SR-Flip Flop

 
 


S	R	Q	\bar{Q}
0	0	Q	Q
1	0	1	0
0	1	0	1
1	1	0	0

  

S	R	Q	\bar{Q}
1	1	Q	Q
0	1	1	0
1	0	0	1
0	0	1	1



JK- Flip Flop

  



J_n	K_n	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	\bar{Q}_n

(c)

Other Flip-Flops

 
 


Toggle Flip-Flop

  


Delay Flip-Flop

Race Problem

 
 


Signal can race around during $\phi = 1$

Master-Slave Flip-Flop


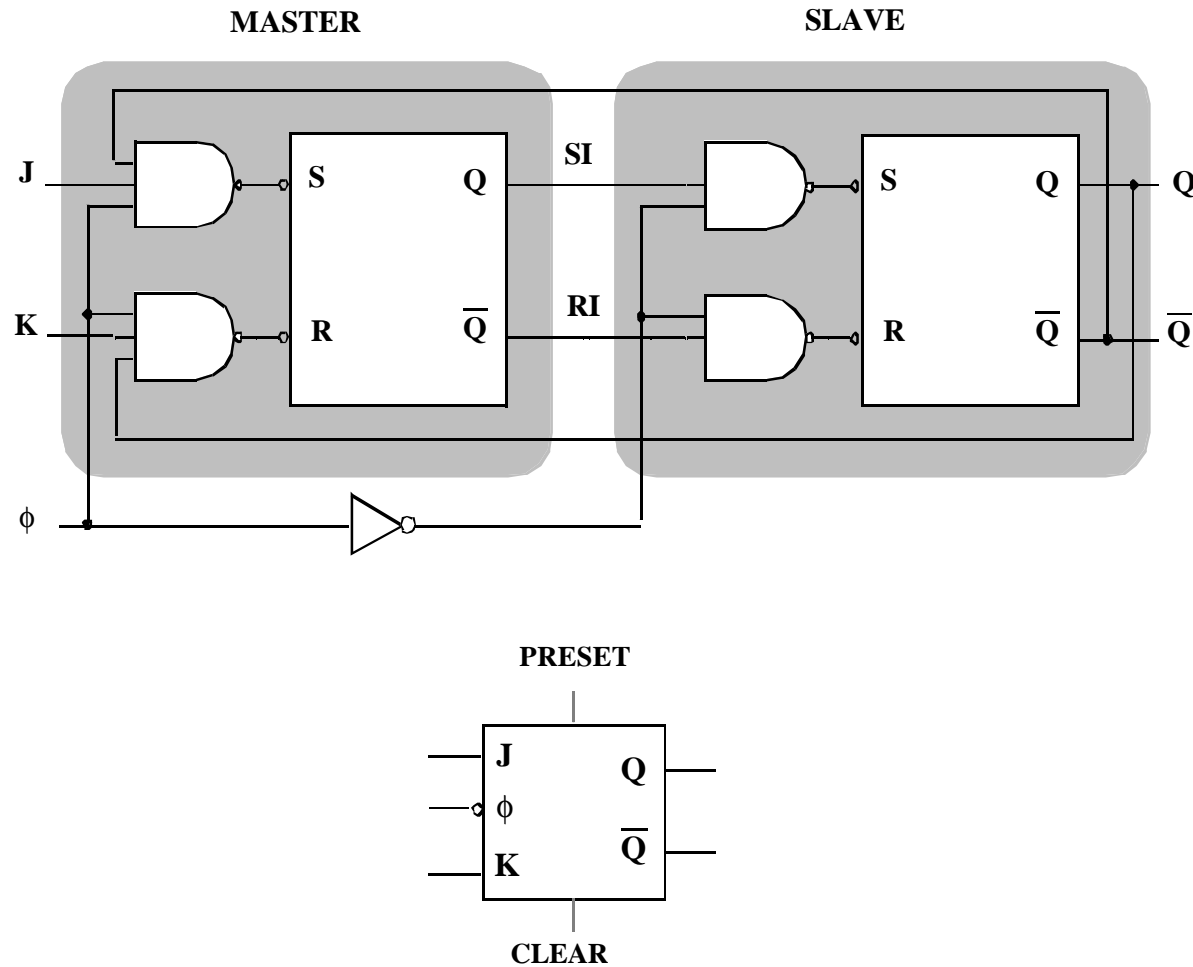


Propagation Delay Based Edge-Triggered

  


= Mono-Stable Multi-Vibrator


Edge Triggered Flip-Flop

 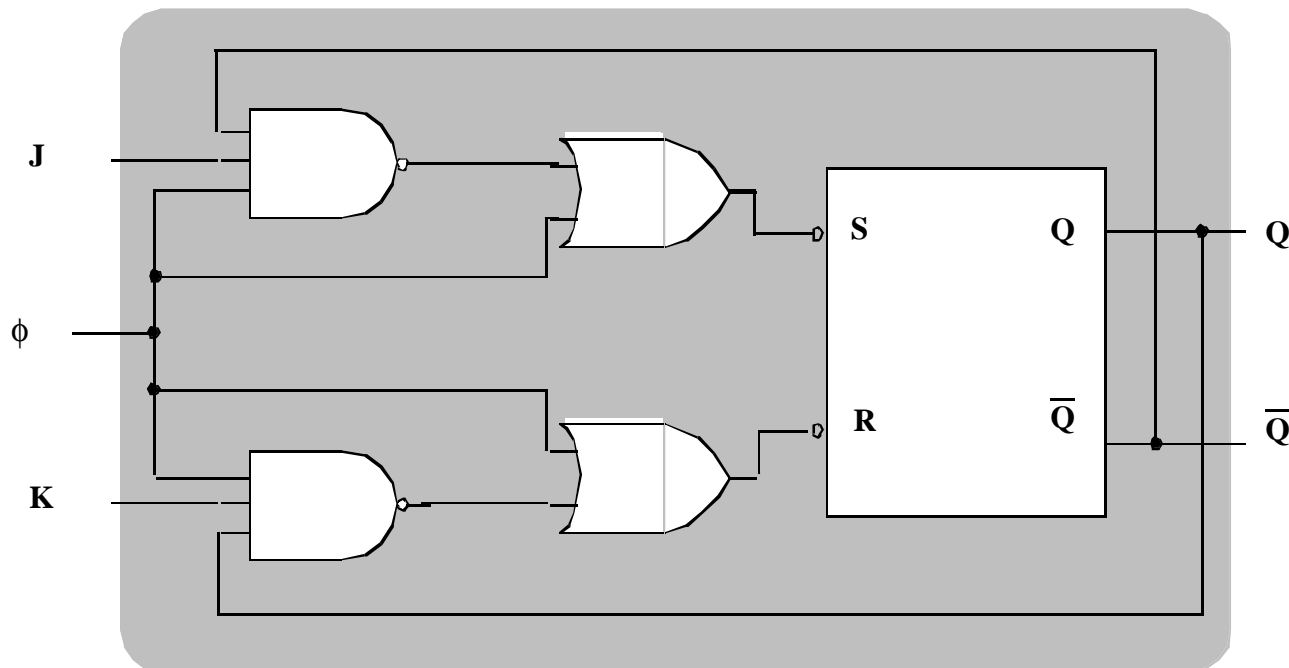

Flip-Flop: Timing Definitions

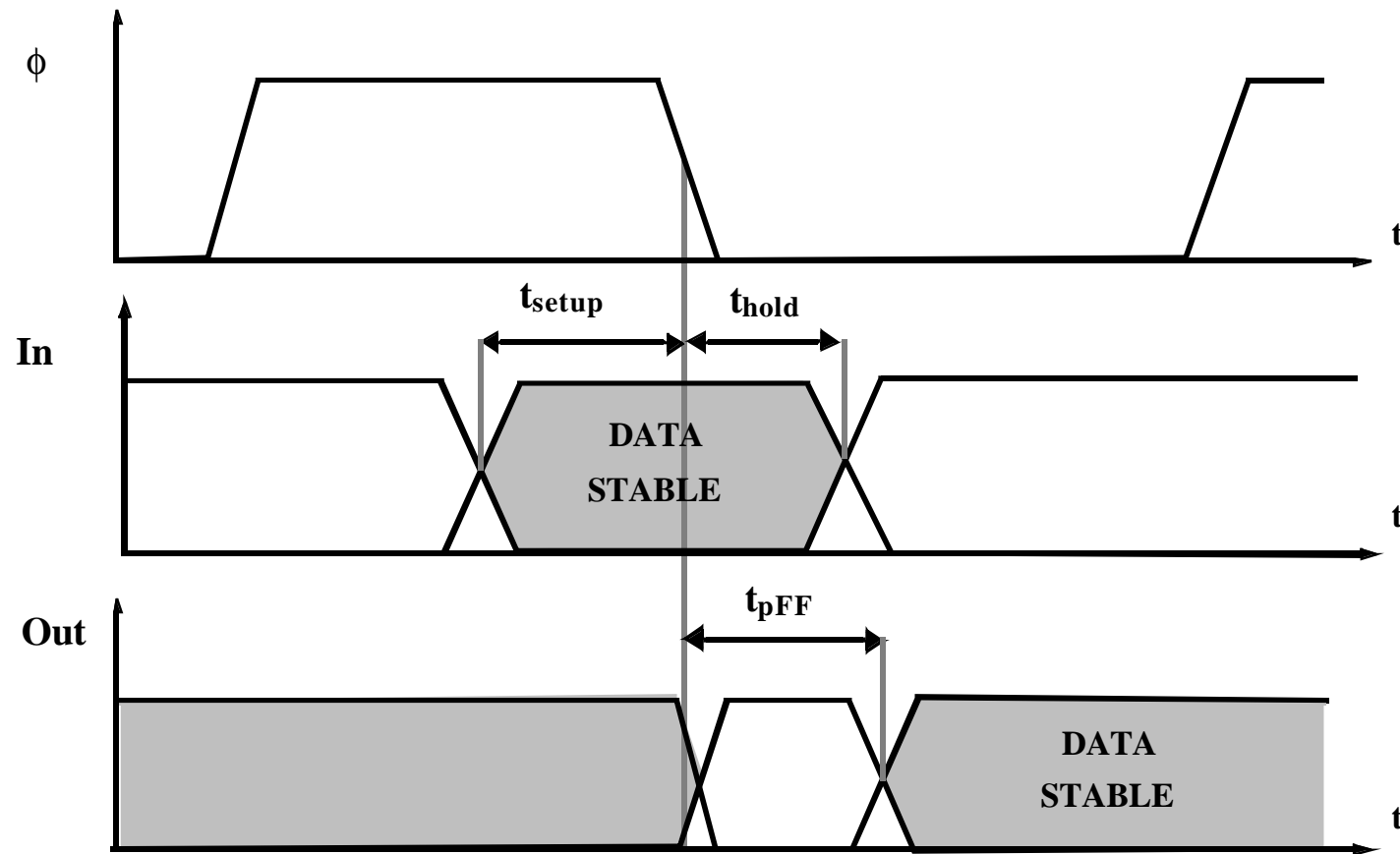


Maximum Clock Frequency

 


$$t_{pFF} + t_{p,comb} + t_{setup} < T$$


CMOS Clocked SR- FlipFlop

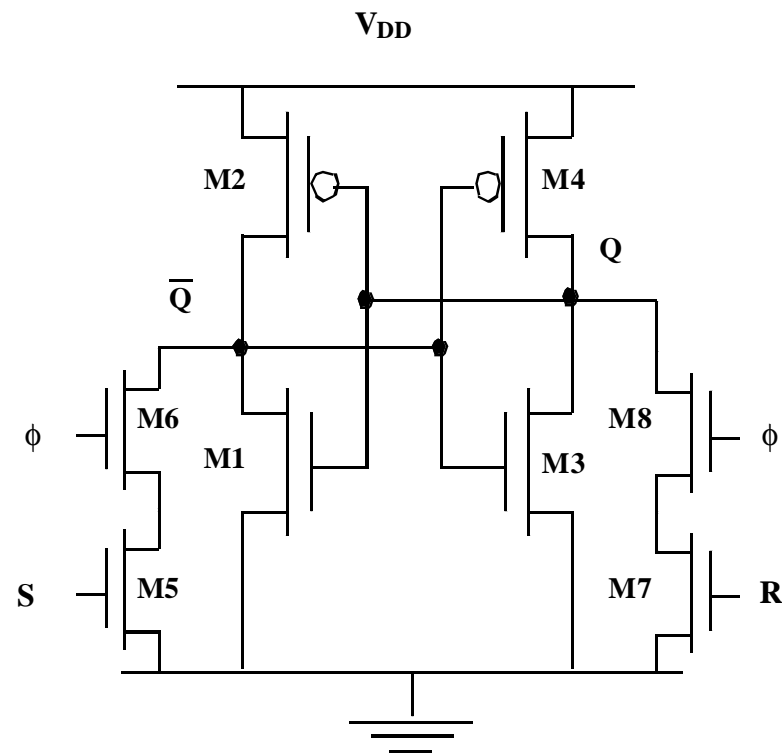


Flip-Flop: Transistor Sizing

 


6 Transistor CMOS SR-Flip Flop

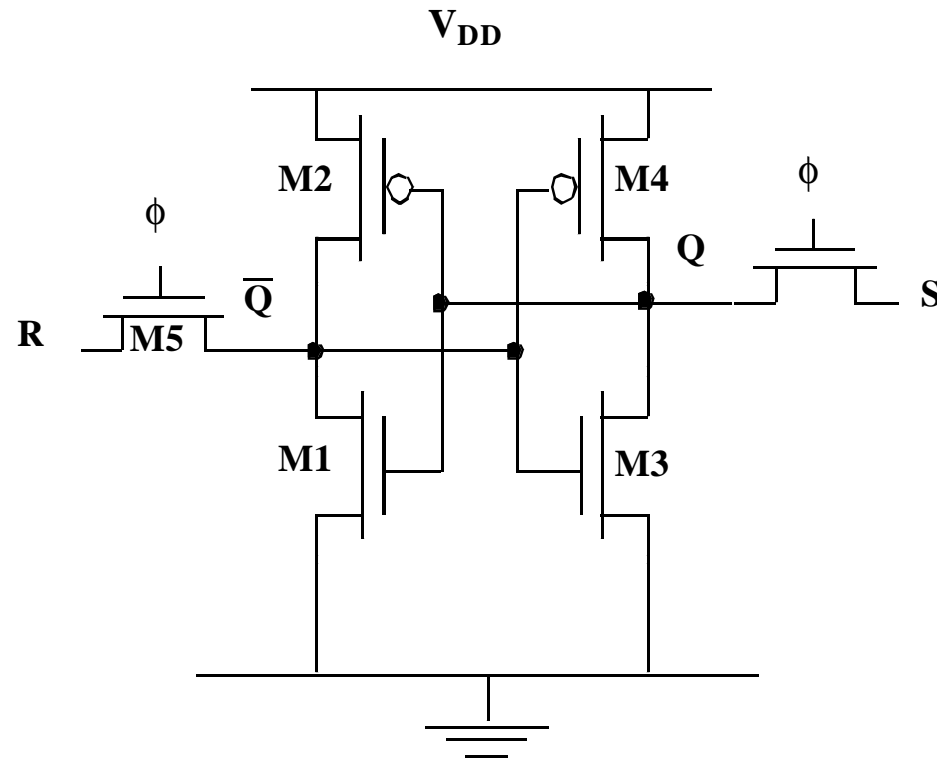

Charge-Based Storage

 


(a) Schematic diagram

 

(b) Non-overlapping clocks

Pseudo-static Latch



Master-Slave Flip-Flop

 


Overlapping Clocks Can Cause

- **Race Conditions**
- **Undefined Signals**


2 phase non-overlapping clocks

  

2-phase dynamic flip-flop

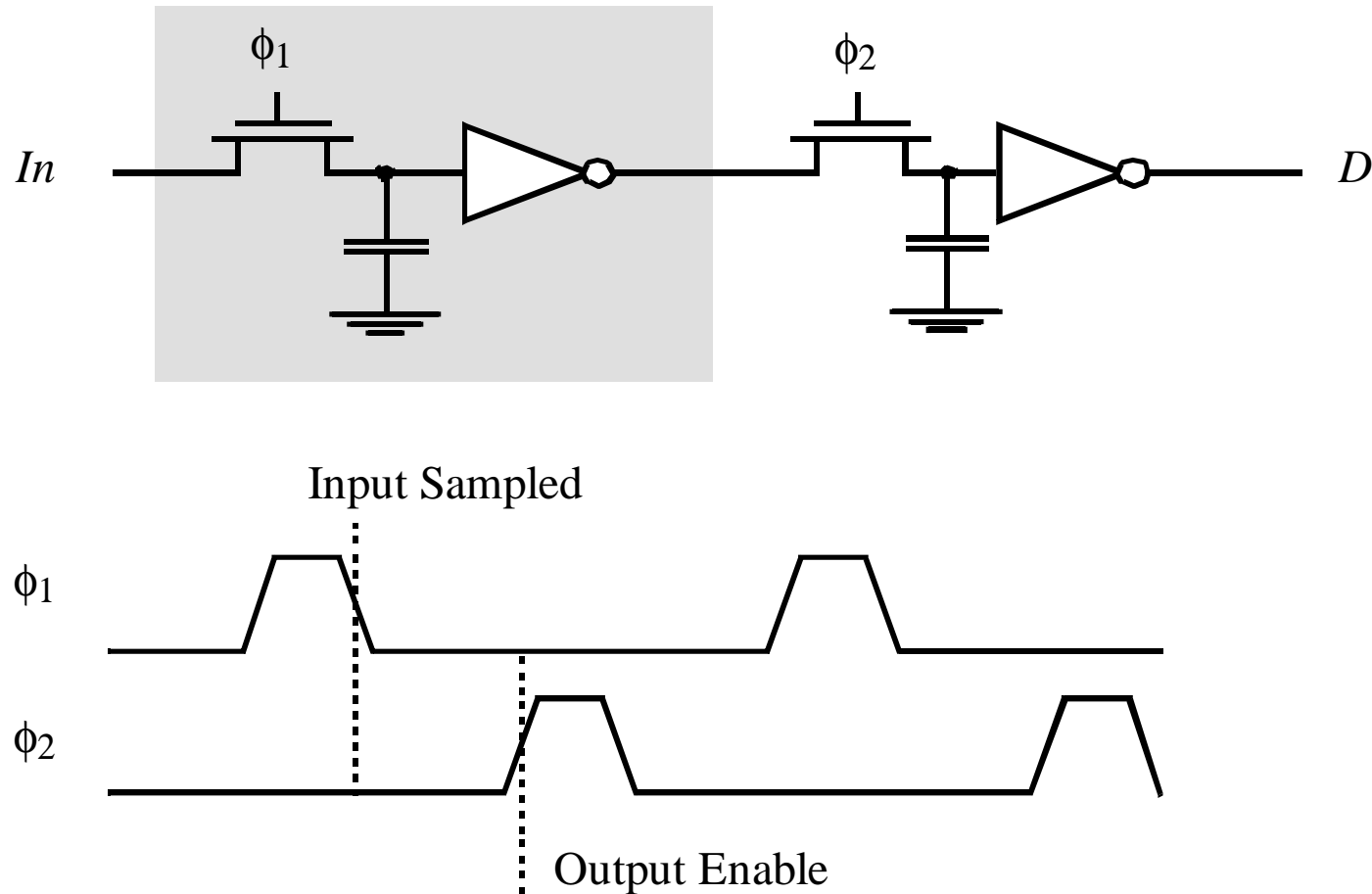


Flip-flop insensitive to clock overlap

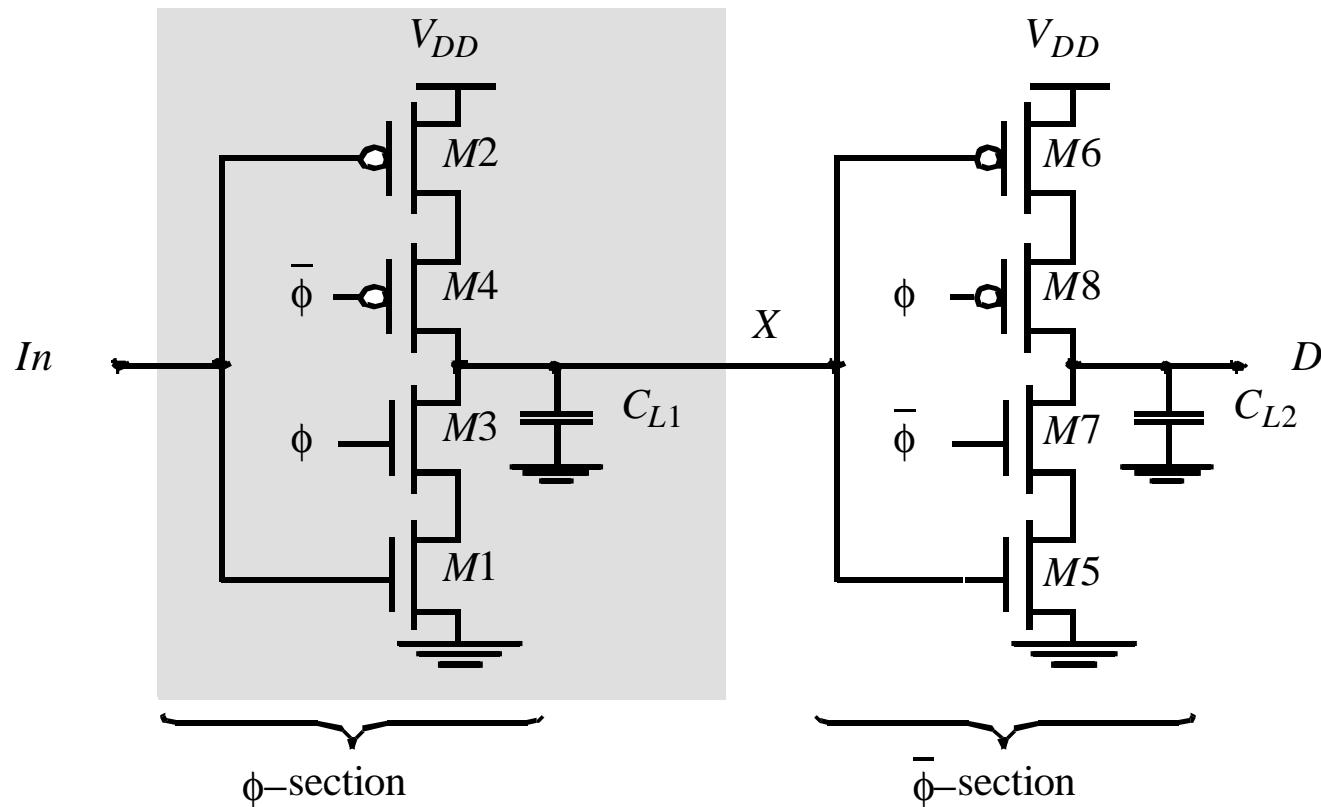


C²MOS LATCH

C²MOS avoids Race Conditions


 


(a) (1-1) overlap

 


(b) (0-0) overlap

Pipelining

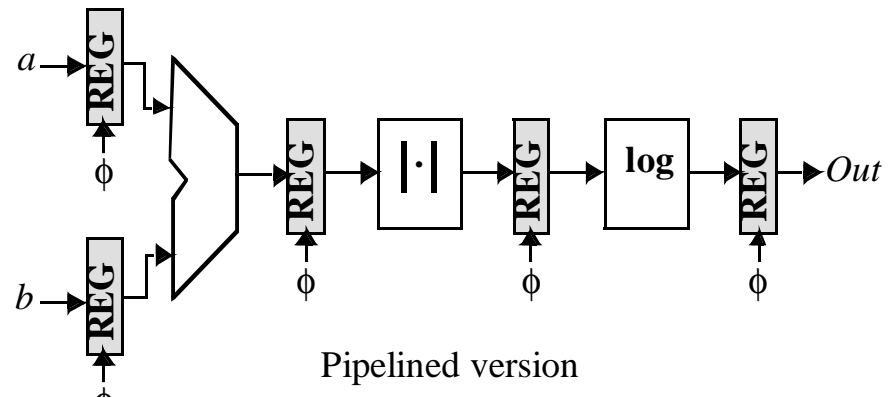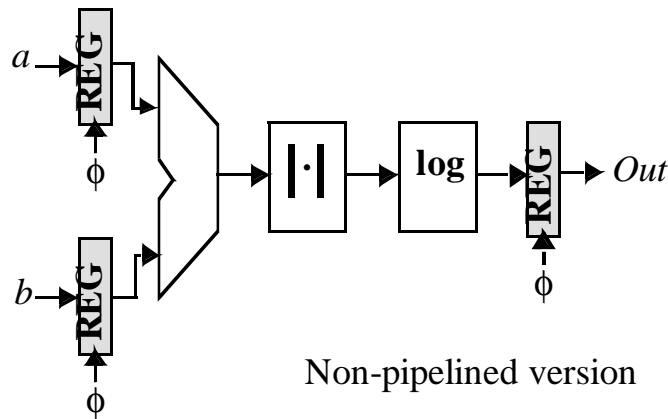

Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log(a_2 + b_2)$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log(a_3 + b_3)$


Pipelined Logic using C²MOS

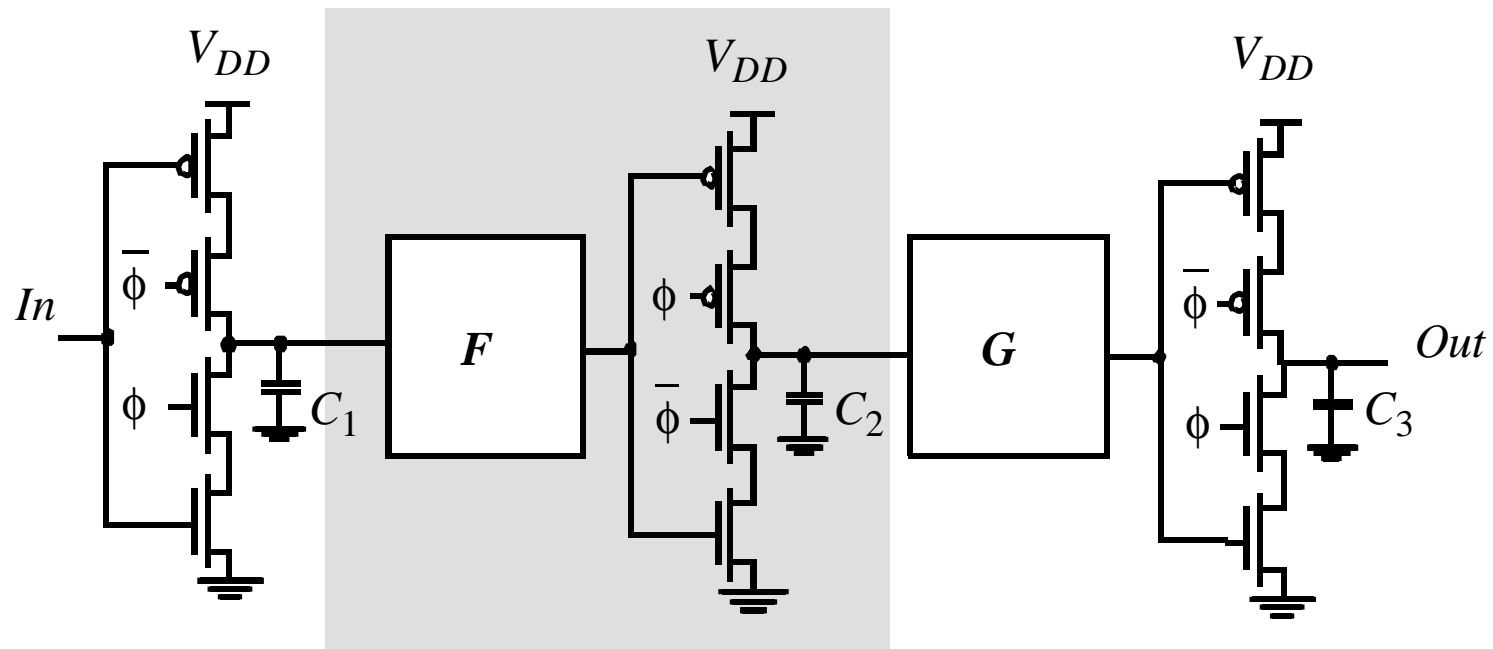

NORA CMOS


What are the constraints on F and G ?

Example

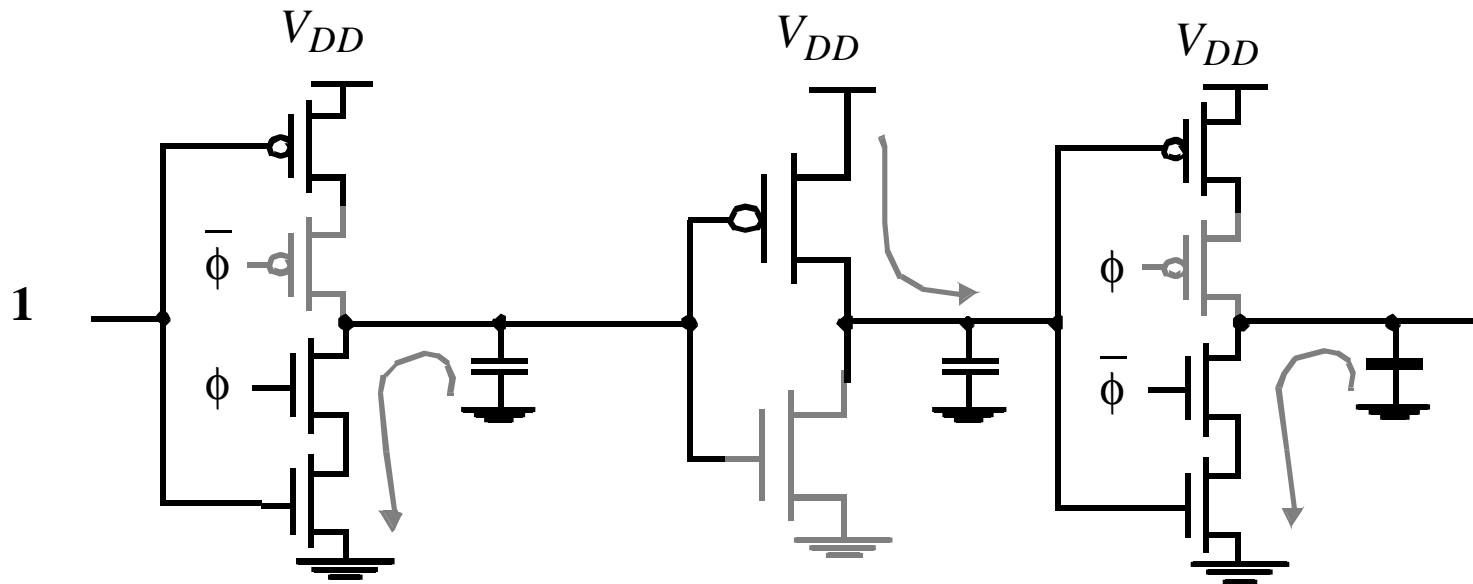


Number of a static inversions should be even


NORA CMOS Modules

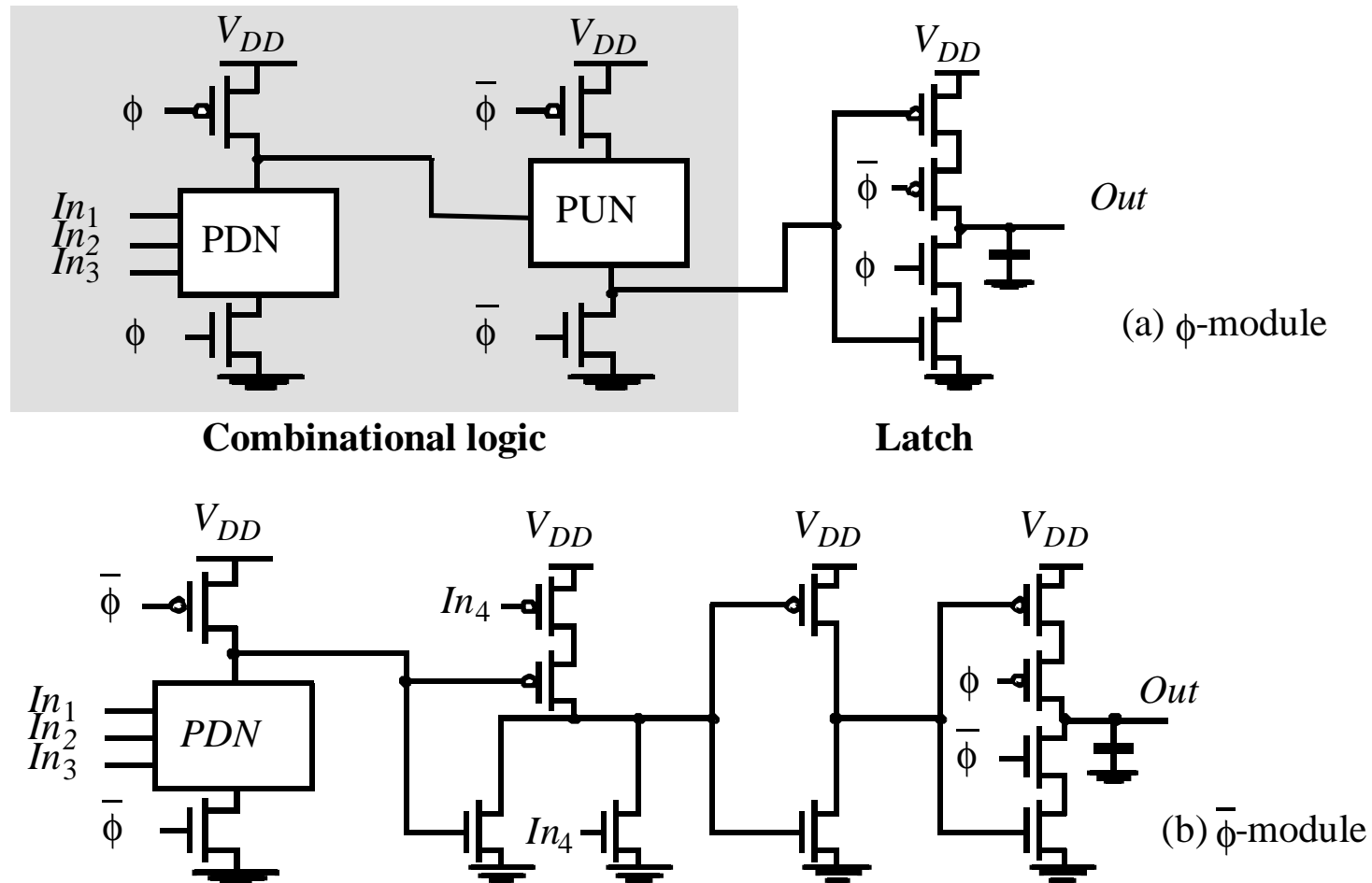

Doubled C²MOS Latches

 


Doubled n-C²MOS latch

 

Doubled n-C²MOS latch


TSPC - True Single Phase Clock Logic

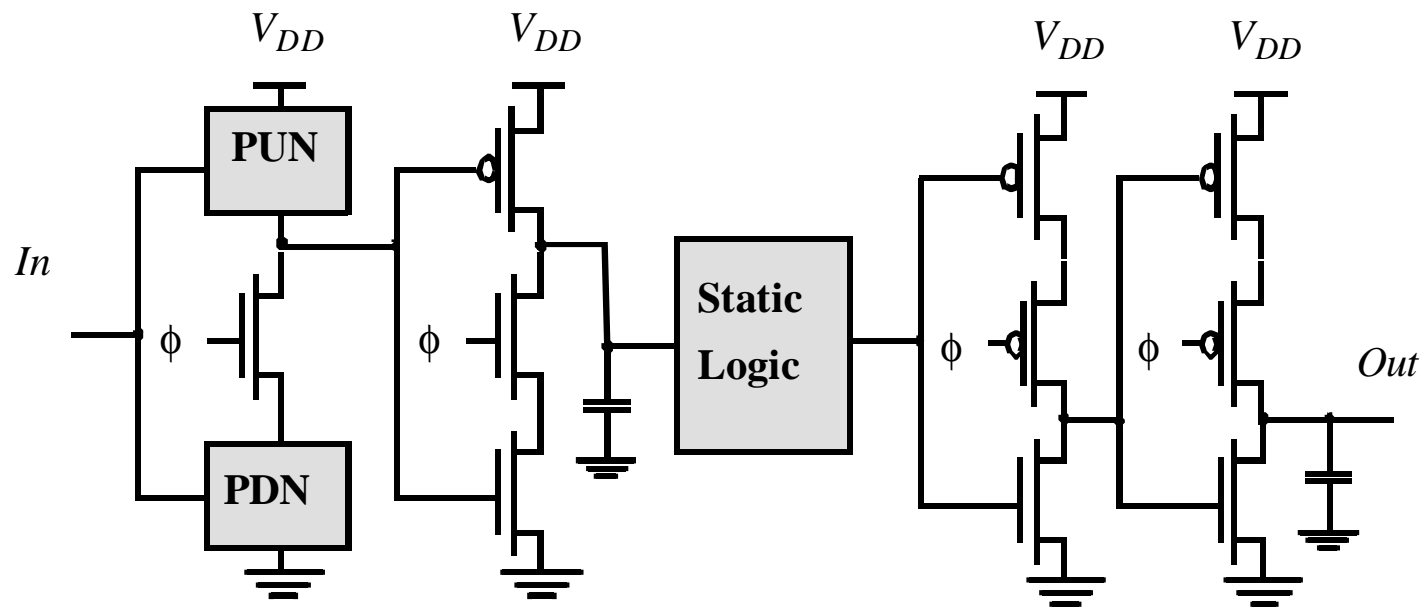


Including logic into
the latch

Inserting logic between
latches


Master-Slave Flip-flops

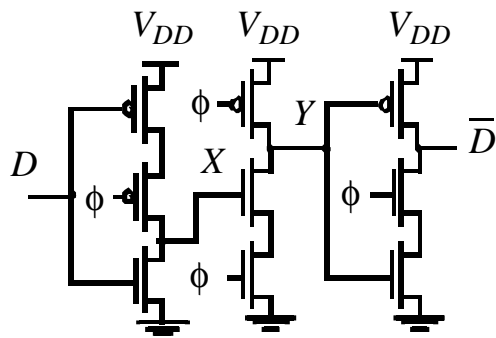

(a) Positive edge-triggered D flip-flop

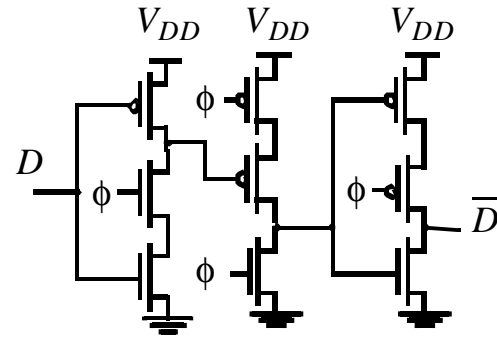


(b) Negative edge-triggered D flip-flop

 


(c) Positive edge-triggered D flip-flop
using split-output latches


Schmitt Trigger

 

 
- **VTC with hysteresis**
- **Restores signal slopes**





Noise Suppression using Schmitt Trigger

 

CMOS Schmitt Trigger

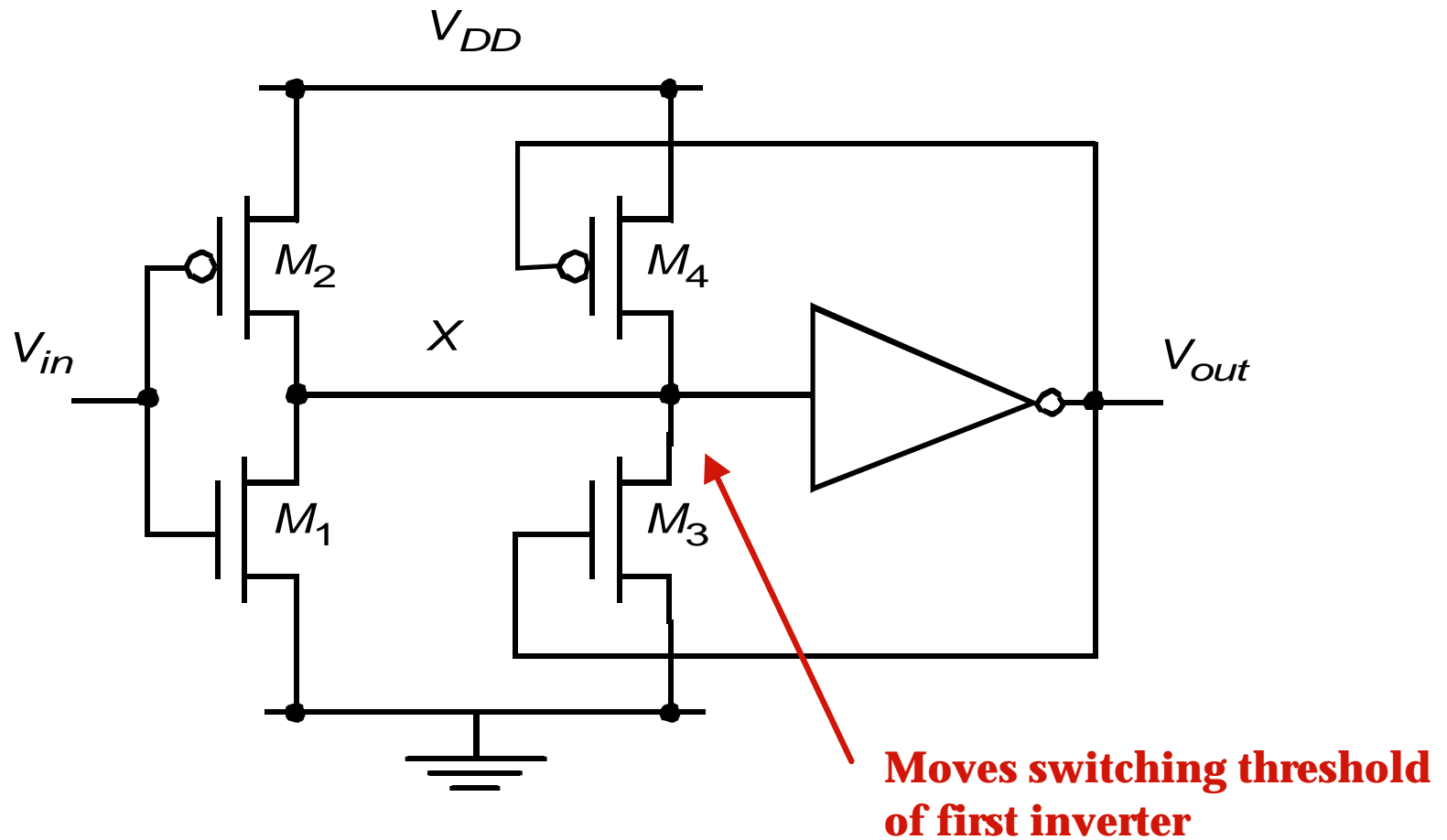


Schmitt Trigger Simulated VTC

  





Multivibrator Circuits

 

 Bistable Multivibrator
flip-flop, Schmitt Trigger




Monostable Multivibrator
one-shot

 


Astable Multivibrator
oscillator


Transition-Triggered Monostable

 

Monostable Trigger (RC-based)

 


(a) Trigger circuit.

 


(b) Waveforms.

Astable Multivibrators (Oscillators)


 


Ring Oscillator

 


simulated response of 5-stage oscillator

Voltage Controller Oscillator (VCO)

 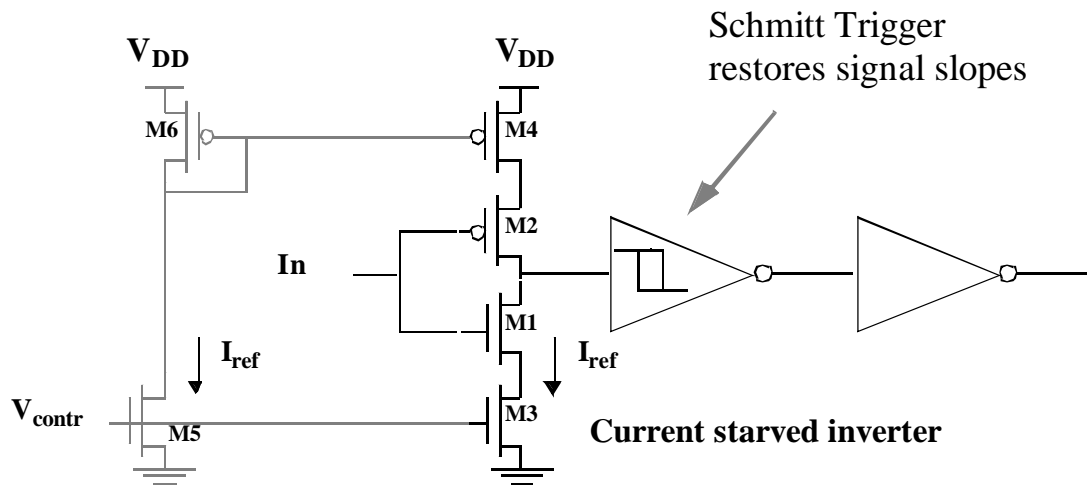

propagation delay as a function of control voltage

Relaxation Oscillator

 

$$T = 2 (\log 3) RC$$