

First name \_\_\_\_\_ **LAST NAME** \_\_\_\_\_

**LAB Session (Circle one):**

Mon 2-5

Tues 2 – 5

Wed 2-5

Thurs 11 - 2

**MIDTERM 2 (Version 1):**

1. Write your name above. **Circle your lab session!**  
**Circle the wrong session or Not circle it, 1 point will be deducted from total score.**
2. **One-side A4-sized note sheet is allowed.**
3. **No Calculator and electronic device** (computer, smart/cell phone, ...) **is allowed**
4. To receive credit, show all your work clearly and readably. Write only answer gets 0
5. There are 6 pages in this exam.
6. Do not write multiple answers, otherwise, the wrong one will be graded.
7. Ask if you have any questions or confusion.

Problem	Score	Your score
1	30	
2	25	
3	45	
Total	100	

1. (30 points)


**1a) (12 pts)** Convert the given decimal numbers to **7-bit two's complement binary numbers** and add them. Then indicate whether the sum overflows or not.

Overflow? (circle one) and explain your reason below:      Yes      No

$$(-37) + (-31)$$


**1b) (8 pts)** Consider the register file timing diagram shown below, answer the questions.

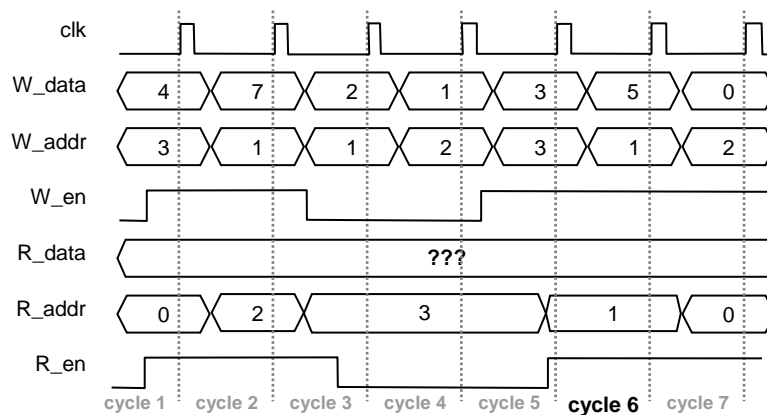1b.1) What is the value of **R\_data** in cycle 6? \_\_\_\_\_



1b.2) If this is a **16x16** register file, how many bits for W\_addr and R\_addr? \_\_\_\_\_ bits

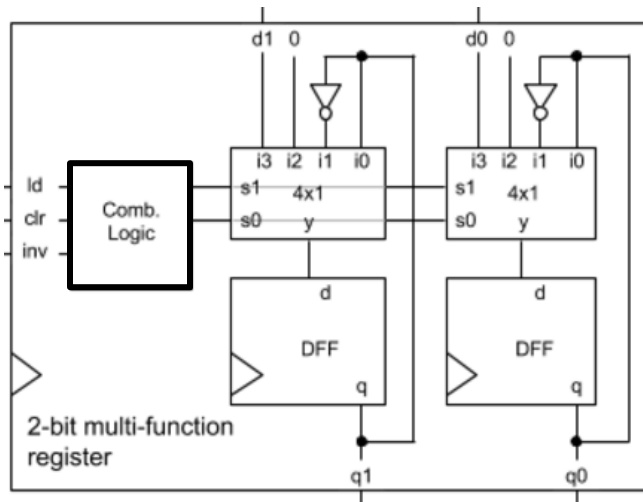**1c) (10 pts)** Given the following circuit and incomplete functional table



clr	ld	inv	s1	s0	Operation
1	x	x			Clear ( $q_1q_0 = 00$ )
0	1	x			Parallel Load
0	0	1			Invert bits
0	0	0			Maintain


x – don't care

1c.1 (4 pts) Complete (write values of s1, s0) in the functional table above

1c.2) (6 pts) Find combinational logic circuit

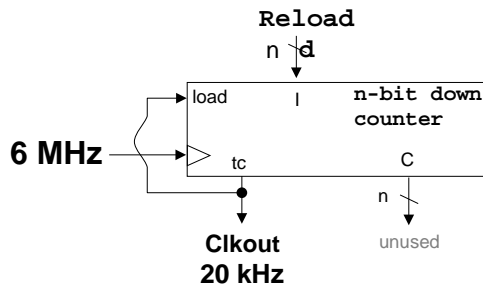2) (25 pts) Counter and its application

**2a) (13 pts)** Given the following circuit, if the frequency of **Clkout** is **20 kHz**,



2a.1) What **value** should be used for **Reload**?

2a.2) What is the *minimum* value of **n** (minimum of bit-width needed for the counter to work as specified)?

**2b) (12 pts)** Given the following Verilog code for ClkDiv, the **Clk input is connected to a 100M Hz (100\*10<sup>6</sup> Hz)** – pin E3 on the Nexys 4 board used in the lab, answer the following questions.

Note: The period (or cycle) of 100 MHz is 0.01us = 0.01\*10<sup>-6</sup> sec

```

`timescale 1ns / 1ps
module ClkDiv(Clk, Rst, ClkOut);
  input Clk, Rst;
  output reg ClkOut;

  parameter DivVal = 250000;
  reg [18:0] DivCnt;
  reg ClkInt;

  always @(posedge Clk) begin
    if( Rst == 1 )begin
      DivCnt <= 0;
      ClkOut <= 0;
      ClkInt <= 0;
    end
    else begin
      if( DivCnt == DivVal ) begin
        ClkOut <= ~ClkInt;
        ClkInt <= ~ClkInt;
        DivCnt <= 0;
      end
      else begin
        ClkOut <= ClkInt;
        ClkInt <= ClkInt;
        DivCnt <= DivCnt + 1;
      end
    end
  end
end
endmodule

```

2b.1) What is the **frequency (in Hz)** of the **ClkOut** signal?

ClkOut has \_\_\_\_\_ Hz

2b.2) If we want to create a **ClkOut signal with frequency of 20k Hz**, what is the correct value of DivVal?

Note: Clk input has 100MHz frequency.


**READ ME: For problem 3, choose 1 problem to complete**(Pick one: Problem **3a** or **3b**)

10 bonus points if you can complete both 3a and 3b with 100% correct answers

3a (45 points) Design a circuit that has four 8-bit unsigned inputs and 1-bit output S that is


$S = 1$  if

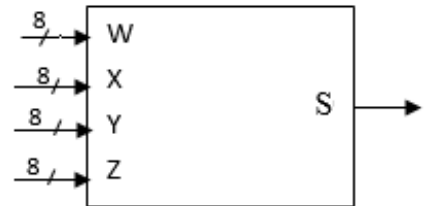$\max(W, X, Y, Z) - \min(W, X, Y, Z)$  is between 39 and 81 (inclusive),  
otherwise  $S = 0$ .



Clearly connect all components, indicate bit-width of each wire, write sufficient details in every component in your circuit.

 *You have the following datapath components available (unsigned only) – decoders, encoders, muxes (any size), 8-bit adder, 8-bit subtractor, 8-bit magnitude comparator, 8-bit MinMax shown below, and any logic gates (and, or, not) with any input numbers.*



Note:


*MinMax* circuit has two 8-bit inputs A and B and two 8-bit outputs  
Min (= minimum between A and B) and  
Max (= maximum between A and B)

**READ ME: For problem 3, choose 1 problem to complete**(Pick one: Problem **3a** or **3b**)

10 bonus points if you can complete both 3a and 3b with 100% correct answers

3b) (45 points) Design a 4-bit up/down-counter that has the following control inputs:

 - clear resets the count to 0,
- set\_val sets the counter to 7,
- left\_shift shifts a counter value to the left by up to 3 bits,
- cnt\_up enables counting up, and
- cnt\_down enables counting down



The counter has 4-bit “C” as the counter output and 1 bit terminal count (tc) output. Control inputs and counter outputs are shown in the block diagram. The **order of operation from highest to lowest priority** is clear, set\_val, left\_shift, cnt\_up, and cnt\_down. When all control inputs are 0, the circuit maintain its content.

When the operation mode is left\_shift, the amount of shift is determined by the state of the cnt\_up and cnt\_down as shown in the table. For example, if left\_shift = 1, cnt\_up cnt\_down = 10 (2 in decimal), the counter value is shifted to the left by 2 bits

left_shift	cnt_up	cnt_down	shift amount
1	0	0	0
1	0	1	1
1	1	0	2
1	1	1	3

Clearly connect all components, indicate bit-width of each wire, write sufficient details in every component in your circuit.

You have **ONLY** the following datapath components available (unsigned only):

decoders, encoders, muxes (any size), 4-bit parallel load register, 4-bit adder, 4-bit subtractor, 4-bit magnitude comparator, the 2-bit left shifter with enable (use symbol  $\ll 2$ , if enable = 1, it left- shifts the 4-bit input by two bits, else passes its input to its output without shifting), the 1-bit left shifter with enable ( $\ll 1$ ), and logic gates. Note that there is no 1-bit register available.