

Problems in Old Midterm 1 Exam with Solution

To receive credits show all your work clearly. Write only answer gets 0.

1. Number system and conversion

1a.1) Convert 155 to

a) **Binary** number and

b) **Hexadecimal** number

	128	64	32	16	8	4	2	1
155	1			1	1		1	1
=> binary	= 10011011							
=> Hexadecimal	= 9B							

1a.2) Convert 764 in octal-based number (base-8) to

a) **Binary** number and

b) **Hexadecimal** number

Each octal digit is 3-bit binary

764	111 110 100 (binary)
1F4	(hexadecimal)

1b) Find a **binary number** of a given *decimal* number **456**


1	1	1	0	0	1	0	0
256	128	64	32	16	8	4	2

1c) Find **hexadecimal number** of a given *octal (based-8)* number **6471₈**


6471 = 110100111001 in binary
=> 1101 0011 1001 = **D39** in hexadecimal

2) Given the circuit implemented with transistors, choose (circle) the one that implements the logic 2-input **NOR gate**.


(a)

 


(b)

 

(c)

 

(d)

 

When both x and y are 0, $F = 1$

x	y	$F = (x+y)'$
0	0	1
0	1	0
1	0	0
1	1	0

3) Which of the following is the correct Boolean equation for **output d12 of a 4x16 decoder**?

Note: inputs are in the order $i_3 i_2 i_1 i_0$ and outputs are in the order of $d_{15} d_{14} \dots d_1 d_0$

(a) $d_{12} = i_3 + i_2 + i_1' + i_0$

(b) $d_{12} = i_3 + i_2 + i_1' + i_0'$

(c) $d_{12} = i_3 i_2 i_1' i_0$

(d) $d_{12} = i_3' i_2' i_1 i_0'$

(e) $d_{12} = i_3' i_2' i_1 i_0$

(f) $d_{12} = i_3 i_2 i_1' i_0'$

4) Given a 4x2 **priority encoder** (where **d3 has the highest priority** and inputs are in the order $d_3 d_2 d_1 d_0$), what is the output of e_1 and e_0 given that $d_0 = 1$, $d_1 = 0$, **$d_2 = 1$** , $d_3 = 0$.

(a) $e_1 = 0$, $e_0 = 0$

(b) $e_1 = 0$, $e_0 = 1$

(c) **$e_1 = 1$, $e_0 = 0$**

(d) $e_1 = 1$, $e_0 = 1$

(e) The output is unknown since the input combination is invalid for a priority encoder.

5) Given $F(a, b, c) = ac + b'c$, which of the following is the **inverse of F**?

(a) $F' = c'$

(b) $F' = a'c' + b$

(c) **$F' = a'b + c'$**

(d) $F' = a'c' + bc'$

(e) $F' = a'b + c$

(f) None of the above

$F' = (ac + b'c)' = (ac)' \cdot (b'c)'$

$= (a' + c')(b + c')$

$= a'b + a'c' + c'b + c'$

$= a'b + c'(a' + b + 1)$

$= a'b + c'$

6) Given the following logic equation

$$F = A'B' + A'BC' + B'C + A(B+C)'$$

Minimize/Simplify using only Boolean algebra.


$$\begin{aligned} F &= A'B' + A'BC' + B'C + AB'C' \\ &= A'(B' + BC') + B'(C + AC') \\ &= A'(B' + C') + B'(C + A) \\ &= A'B' + A'C' + B'C + B'A \\ &= A'B' + AB' + A'C' + B'C \\ &= B' + B'C + A'C' \\ &= B'(1 + C) + A'C' \\ &= B' + A'C' \end{aligned}$$

Double check using K-map

	BC			
A	00	01	11	10
0	1	1		1
1	1	1		

=> $F = B' + A'C'$

 7) Given the following circuit using **3x8 decoder** and **4-input OR gate**, write the Boolean equation/expression in a **sum-of-minterm** form.



$$F = d1 + d2 + d4 + d5$$

i2	i1	i0		from 3x8 decoder	F
A	B	C			
0	0	0		d0 = 1	0
0	0	1		d1 = 1	1
0	1	0		d2 = 1	1
0	1	1		d3 = 1	0
1	0	0		d4 = 1	1
1	0	1		d5 = 1	1
1	1	0		d6 = 1	0
1	1	1		d7 = 1	0

$$\begin{aligned} F &= d1 + d2 + d4 + d5 \\ &= A'B'C + A'BC' + AB'C' + AB'C \end{aligned}$$

8) Given the following Boolean equation:


$$F(c, d, a, b) = \Sigma(0, 2, 6, 7, 8, 10, 12, 14)$$

8a) Use Karnaugh-map to find its **minimal** sum-of-product form.

$cd \backslash ab$	00	01	11	10
00	1			1
01			1	1
11	1			1
10	1			1

$$F = c'da + cb' + d'b'$$

 8b) Implement the given equation $F(c, d, a, b)$ using 4x1 MUX with signals a and b connecting to select lines S1 and S0, respectively.



From K-map above, look at one column at a time. Why?

Look at **1st column**, when $ab = 00$, use $ab = 00$ in 4x1 mux above, $F = i0$ (from mux)

From first coln,

$c \backslash d$	0	1
0	1	0
1	1	1

$\Rightarrow c + d'$

Therefore, the circuit at $i0$ is $c + d'$

Look at **2nd column**, when $ab = 01$, use $ab = 01$ in 4x1 mux above, $F = i1$ (from mux)

Since value from the 2nd column are all logic 0, the circuit (or logic) at $i1$ is 0

Look at **4th column**, when $ab = 10$, use $ab = 10$ in 4x1 mux above, $F = i2$ (from mux)

Since value from the 4th column are all logic 1, the circuit (or logic) at $i2$ is 1

Look at **3rd column**, when $ab = 11$, use $ab = 11$ in 4x1 mux above, $F = i3$ (from mux)

the circuit (or logic) at $i3$ is $c'd$

9) Write the **simplified/minimized sum-of-products** form for F using **K-map**

$$F = (x + y + w')(x' + y' + z)(x' + w + z')$$


From F, the term $(x + y + w') = 0$ when $x = 0, y = 0$ and $w = 1$

the term $(x' + y' + z) = 0$ when $x = 1, y = 1$ and $z = 0$


the term $(x' + w + z') = 0$ when $x = 1, w = 0$ and $z = 1$

	wz				
xy	00	01	11	10	
00	1	1	0	0	Group the terms with 1, then $F = x'y + x'w' + xwz + xy'z'$
01	1	1	1	1	
11	0	0	1	0	
10	1	0	1	1	

 
10) Given a digital circuit below, implement the circuit above using **only 2-input NAND gates**. Eliminate unnecessary NAND gates.



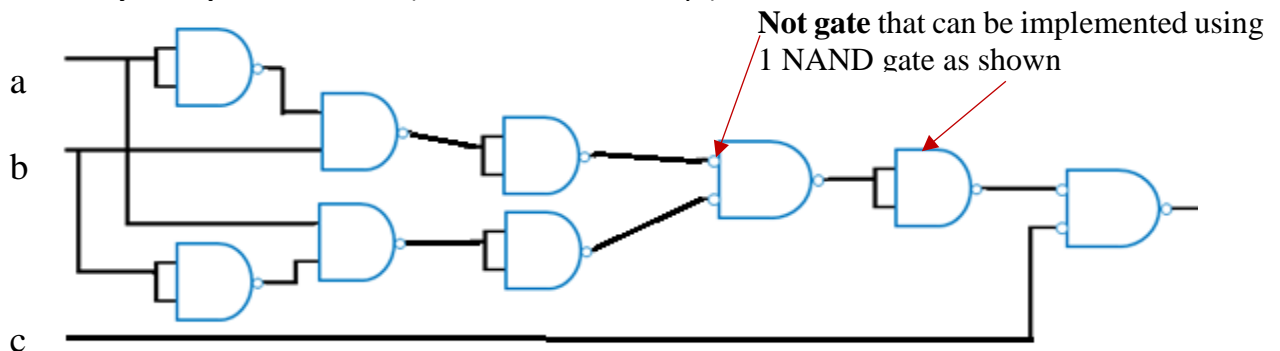One way of implementations (there are several ways)



Eliminate unnecessary NAND gates

 

11) Using the combinational logic design process, design a circuit with two 2-bit inputs (A and B) and one 2-bit output (M). Your circuit should output the **minimum** of the two input values. For example,

- A = $a_1a_0 = 10$ and B = $b_1b_0 = 11$, then M = $m_1m_0 = 10$
since $10 (= 2 \text{ in decimal}) < 11 (= 3 \text{ in decimal})$
- A = $a_1a_0 = 11$ and B = $b_1b_0 = 01$, then M = $m_1m_0 = 01$
- A = 10 and B = 10, then M = 10 since both inputs are the same value

Your answers must include

a) **Truth table**

b) **minimized** sum-of-products form for the outputs

a1	a0	b1	b0	m1	m0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	0	1
1	0	0	0	0	0
1	0	0	1	0	1
1	0	1	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	1	0
1	1	1	1	1	1

For m1,

	b1b0			
a1a0	00	01	11	10
00				
01				
11			1	1
10			1	1

Group the terms with 1, then

$$\mathbf{m1 = a1b1}$$


For m0,

	b1b0			
a1a0	00	01	11	10
00				
01			1	1
11		1	1	
10		1		

Group the terms with 1, then

$$\mathbf{m0 = a0b0 + a1'a0b1 + a1b1'b0}$$

 12) Consider four seats arranged in a circle and described by **Boolean variables** i_0 to i_3 .



Boolean variable i_0 is true ($=1$) if seat 0 is occupied and i_0 is false if the seat is not occupied (no one is sitting in the seat), likewise for i_1 , i_2 , and i_3 .

a) Write a **truth table that is true ($F = 1$) if at least two people are sitting next to each other and at least one seat is not occupied.**

b) Simplify your design using K-map. Write the expression/equation in minimal sum-of-product form.

Inputs				Output
i_0	i_1	i_2	i_3	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	1
0	1	0	0	
0	1	0	1	
0	1	1	0	1
0	1	1	1	1
1	0	0	0	
1	0	0	1	1
1	0	1	0	
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	

K-map

$i_0 i_1 \backslash i_2 i_3$	00	01	11	10
00			1	
01			1	1
11	1	1		1
10		1	1	

$$F = i_0 i_1 i_2' + i_0 i_1' i_3 + i_0' i_2 i_3 + i_1 i_2 i_3'$$

- 13) A “2-bit” comparator circuit receives two 2-bit numbers, $A = A_1A_0$, and $B = B_1B_0$. Design this comparator that produces an output $F = 1$ if $A \geq B$. Write its minimum sum-of-product form.

$A_1A_0 \backslash B_1B_0$	00	01	11	10
00	1			
01	1	1		
11	1	1	1	1
10	1	1		1


$$F = \mathbf{B1'B0'} + A0B1' + \mathbf{A1B1'} + A1A0 + \mathbf{A1B0'}$$

- 14) Given the following circuit,


a) write its *minimized sum-of-products form* for F

	cd			
ab	00	01	11	10
00	1	1	1	1
01		1		
11			1	
10	1		1	1

 Group the terms with 1, then
 $\mathbf{F = b'd' + a'c'd + acd + b'c}$
Or
 $\mathbf{F = b'd' + a'c'd + acd + a'b'}$




 - b) Implement the simplified equation of F from 14a) using 4x1 MUX with signals b and c connecting to select lines S1 and S0, respectively, as shown below.





From the equation in 14a), we can write the following K-map


ad	00	01	11	10
bc 00	1	1		1
01	1	1	1	1
11			1	
10		1		

 

  15) Given a level-sensitive SR Latch with the input pattern below, complete the timing diagram below (draw S1, R1, and Q). Assuming that S1, R1, and Q are initially 0 and the logic gates have a *very small* nonzero delay.



 
16) Given the following waveform where C and D are inputs and the rest are outputs, which output waveform (Q1, Q2, Q3, Q4, or Q5) belongs to



D-FF using rising edge of Clk

Q3

Choose one of Q1, Q2, Q3, Q4, Q5

 


Note: **C** and **D** in the **above waveform** are connected to **Clk** and **D**, respectively of this flip-flop.

D-latch with the function table below



Q4

Choose one of Q1, Q2, Q3, Q4, Q5

 


Note: **C** and **D** in the **above waveform** are connected to **C** and **D**, respectively of this latch.

  17) Given a level-sensitive SR Latch with the input pattern below, complete the timing diagram below (draw S1, R1, and Q). Assuming that S1, R1, and Q are initially 0




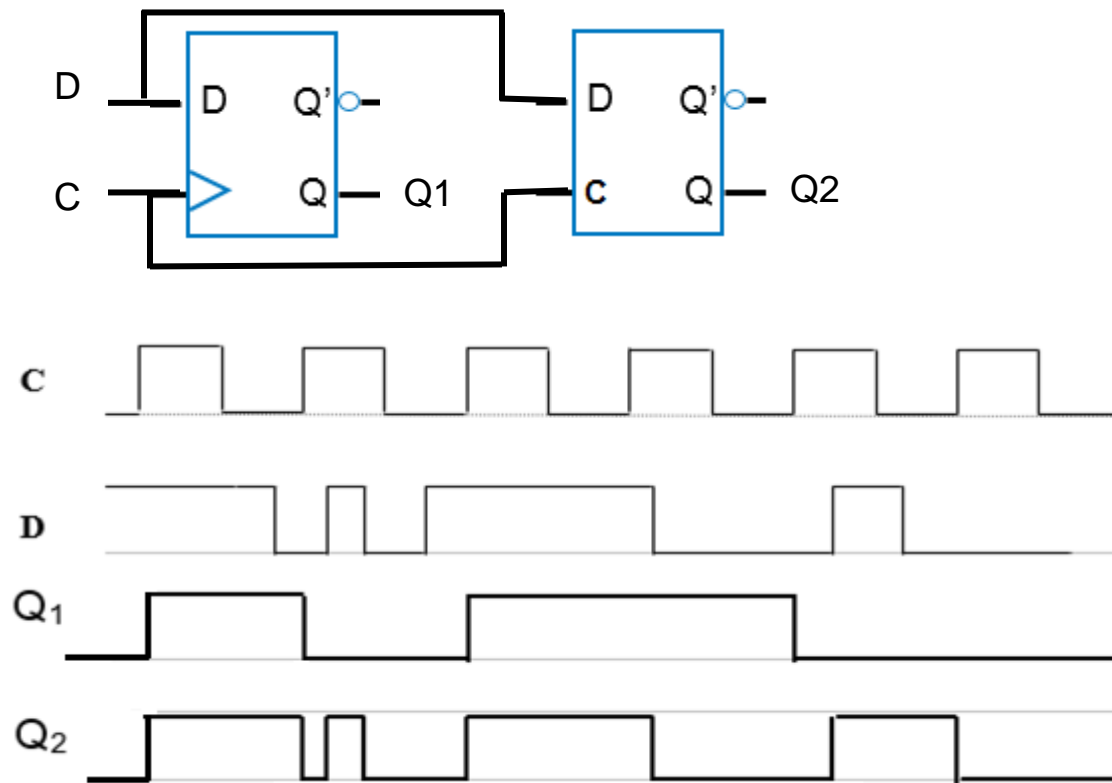18) Trace the behavior of **D-Latch** and **D flip-flop** for the following input patterns. Assume that Q_1 and Q_2 is initially 0 and logic gates have a very small nonzero delay.



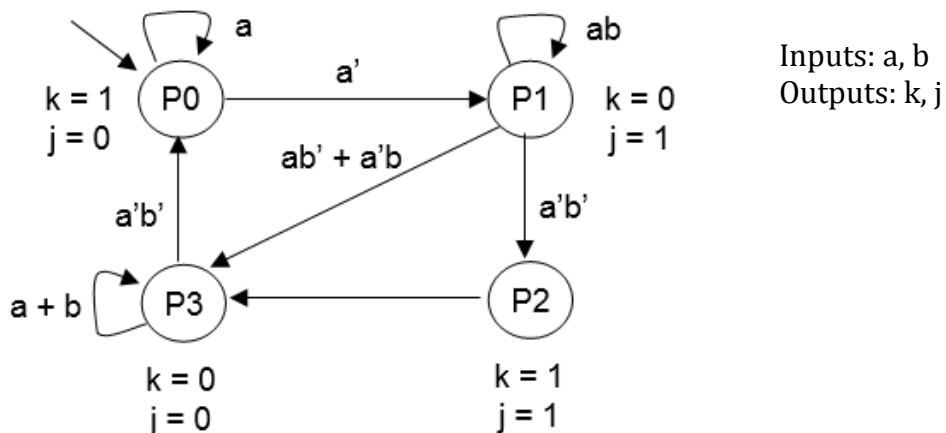19) Using the **sequential logic design process**, convert the provided state diagram (FSM) to **a circuit**. Be sure to label and show each step.

Note: Write the Boolean equations (in minimum sum-of-products form) is sufficient. NO need to draw a circuit.



4 states -> 2 D-FFs (2-bit state) are used. P0 = 00, P1 = 01, P2 = 10 and P3 = 11

S1	S0	a	b	n1	n0
0	0	0	0	0	1
0	0	0	1	0	1
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	1	0
0	1	0	1	1	1
0	1	1	0	1	1
0	1	1	1	0	1
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	1	1
1	0	1	1	1	1
1	1	0	0	0	0
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	1	1

Next state n1 and n0

n1	ab
S1S0	00 01 11 10
00	
01	1 1 1
11	1 1 1
10	1 1 1 1

$n1 = S1S0' + S1b + S0ab' + S1'S0a'$
 or
 $n1 = S1S0' + S1a + S0a'b + S1'S0a'$

n0	ab
S1S0	00 01 11 10
00	1 1
01	1 1 1
11	1 1 1
10	1 1 1 1

$n0 = S0'a' + a'b + S0a + S1a$
 or
 $n0 = S1S0' + S0a + a'b + S0'a'$

S1	S0	k	j
0	0	1	0
0	1	0	1
1	0	1	1
1	1	0	0

Outputs k and j


$$k = s0'$$

$$j = s1's0 + s1s0'$$

20) Design a synchronous sequential circuit of a sequence detector, which has one input b and one output w. It accepts a sequence of bits (one bit (0 or 1) at a time) and outputs w = 1 when the **target sequence 1001** is detected. Non-Overlapping sequence is detected.

a) Draw its **state diagram**

 b) **Minimum of bits** to represent/encode states in your designed state diagram are _____




Minimum of bits to represent/encode states in your designed state diagram are 3

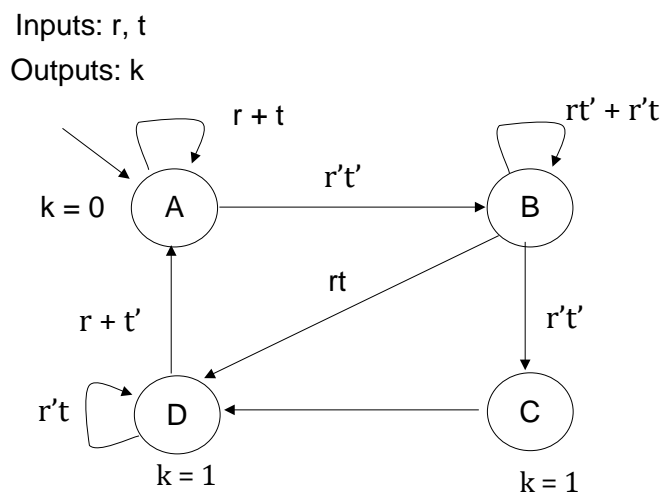- 21)** Using the sequential logic design process, convert the provided state diagram (FSM) to a circuit. Be sure to label and show each step.

Note: Write the Boolean equations (in minimum sum-of-products form) is sufficient.

You DO NOT need to provide a gate-level implementation (no drawing a circuit).



Let A – 00, B – 01, C – 10, D – 11

s1	s0	r	t	k	n1	n0
0	0	0	0	0	0	1
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	1	0
0	1	0	1	0	0	1
0	1	1	0	0	0	1
0	1	1	1	0	1	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	0	0
1	1	0	1	1	1	1
1	1	1	0	1	0	0
1	1	1	1	1	0	0

$$k = s1$$

$$n1 = s1s0' + s1r't + s1's0r't' + s1's0rt$$

s1s0	rt	00	01	11	10
00	0	0	0	0	0
01	1	0	1	0	0
11	0	1	0	0	0
10	1	1	1	1	1

$$n0 = s1s0' + s0r't + s1's0r + s0'r't'$$

s1s0	rt	00	01	11	10
00	1	0	0	0	0
01	0	1	1	1	1
11	0	1	0	0	0
10	1	1	1	1	1

22) Design a vending machine that delivers coffee after depositing 35 cents.

There is a single coin slot for two types of coins, N and D.

D is for dimes (10 cents) and N is for nickels (5 cents).

It does not take other coin types. Single coin slot means that you can insert one coin at a time!


If a dime is deposited, D is 1 and N is 0.

If a nickel is deposited N is 1, D is 0.

N and D cannot be 1 at the same time.


The vending machine does **not** return changes if you deposit more than 35 cents.

 When 35 cents is reached, coffee is served by outputting S as 1 that enables the coffee dripping system. **In the next cycle, the vending machine goes back to the initial state for the next coin input for another coffee.**



a) Draw a state diagram (FSM).

 b) From your state diagram, what are the minimum of bits that your design needs to use for a state register?




b) since there are 8 states, minimum number of bits used for the state register = 3

Note: since ND never occurs, we do not need to draw ND on the state diagram. If you want to include ND in each state, it can be either


- 1) when ND occurs, make it go back to S0. This way, the machine takes the money (all the coins that a buyer has entered so far) if a buyer tries to insert two coins at one time.
- 2) when ND occurs, make it stay at the same state (similar to N'D' case). This way, the machine will still take a buyer money (but only for 15 cents) if a buyer tries to insert two coins at one time.

 23) Given the following simulation waveform for the *sequence detector*.



It has one input b and one output w and its state register uses 2 bits ($state[1:0]$) as shown in the waveform.

 - a) Draw its state diagram (FSM diagram).
- b) What is the target sequence that this detector can detect? (Hint: starting from the initial state (00), find the input sequence such that this detector gives output $w = 1$.)



b) target sequence is 101 (overlapping sequence can be detected)